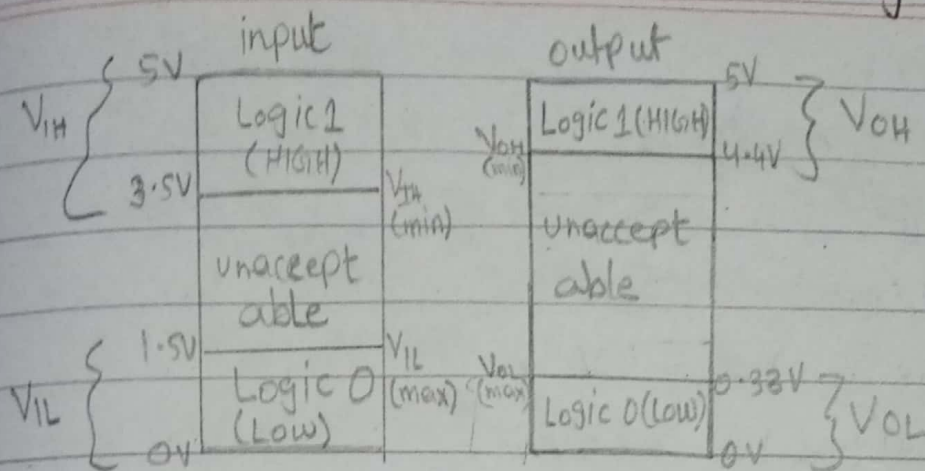



31-05-2021

FLOYD  
Chapter #15

Page #



+5V CMOS

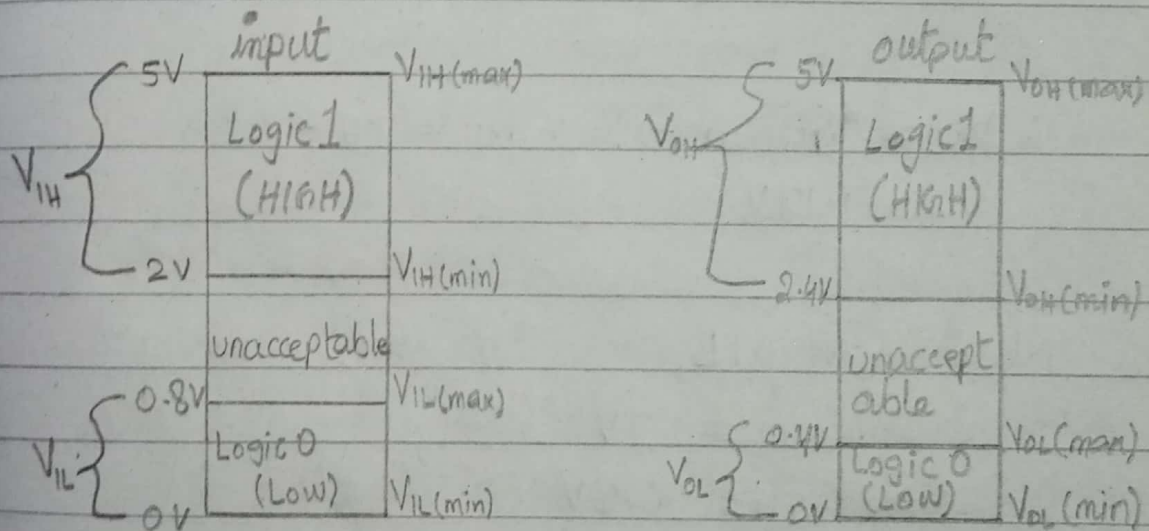

+5V TTL

## Example 15-1

Q. Determine the high-level and low-level noise margins for CMOS and TTL by using the information in figures above.

31-05-2021

Solution:

For 5V CMOS,

$$V_{IH(min)} = 3.5V$$

$$V_{IL(max)} = 1.5V$$

$$V_{OH(min)} = 4.4V$$

$$V_{OL(max)} = 0.33V$$

$$\therefore V_{NH} = V_{OH(min)} - V_{IH(min)} = 4.4 - 3.5$$

$$V_{NH} = 0.9V$$

$$\therefore V_{NL} = V_{IL(max)} - V_{OL(max)} = 1.5 - 0.33$$

$$V_{NL} = 1.17V$$

Now, for TTL,

$$V_{IH(min)} = 2V$$

$$V_{IL(max)} = 0.8V$$

$$V_{OH(min)} = 2.4V$$

$$V_{OL(max)} = 0.4V$$

$$\therefore V_{NH} = V_{OH(min)} - V_{IH(min)} = 2.4 - 2$$

$$V_{NH} = 0.4V$$

$$\therefore V_{NL} = V_{IL(max)} - V_{OL(max)} = 0.8 - 0.4$$

$$V_{NL} = 0.4V$$

Related Problem:

Q. Based on the preceding noise margin calculations, which family of devices, 5V CMOS or TTL, should be used in a high-noise environment?

A. As we calculate the noise immune values of CMOS and TTL; CMOS can immune from more noises as compared to TTL.

Q. Example 15-2

Q. A certain gate draws  $2\mu A$  when its output is HIGH and  $3.6\mu A$  when its output is LOW. What is the avg. power dissipation if  $V_{cc}$  is 5V and gate operated on a 50% duty cycle?

Data:

$$I_{ccH} = 2\mu A = 2 \times 10^{-6} A$$

$$I_{ccL} = 3.6\mu A = 3.6 \times 10^{-6} A$$

$$\text{duty cycle} = 50\%$$

$$V_{cc} = 5V.$$

$$P_D = ?$$



1-06-2021

$$\therefore P_D = V_{CC} I_{CC}$$

$$\therefore I_{CC} = \frac{I_{CCH} + I_{CCL}}{2} = \frac{2 \times 10^{-6} + 3.6 \times 10^{-6}}{2}$$

$$I_{CC} = 2.8 \times 10^{-6} \text{ A}$$

$$P_D = (5)(2.8 \times 10^{-6})$$

$$P_D = 14 \times 10^{-6} \text{ W}$$

Ans.

Related Problem:

Q. A certain IC gate has an  $I_{CCH} = 1.5 \mu\text{A}$  and  $I_{CCL} = 2.8 \mu\text{A}$ . Determine the average power dissipation for 50% duty cycle operation if  $V_{CC}$  is 5V.

Data:

$$I_{CCH} = 1.5 \mu\text{A} = 1.5 \times 10^{-6} \text{ A}$$

$$I_{CCL} = 2.8 \mu\text{A} = 2.8 \times 10^{-6} \text{ A}$$

$$V_{CC} = 5$$

$$P_D = ?$$

Solution:

$$P_D = V_{CC} \cdot I_{CC}$$

$$I_{CC} = \frac{I_{CCH} + I_{CCL}}{2} = \frac{1.5 \times 10^{-6} + 2.8 \times 10^{-6}}{2}$$

2

1-06-2021

Page #

$$I_{cc} = 2.15 \times 10^{-6} \text{ A}$$

$$\text{Now, } P_D = V_{cc} \cdot I_{cc} = (5)(2.15 \times 10^{-6})$$

$$P_D = 10.75 \times 10^{-6} \text{ W}$$

Ans.

Section Checkup 15-1:

Q. Define  $V_{IH}$ ,  $V_{IL}$ ,  $V_{OH}$  and  $V_{OL}$

A.  $V_{IH}$  = Input voltage when HIGH

$V_{OH}$  = Output voltage when HIGH

$V_{IL}$  = Input voltage when LOW

$V_{OL}$  = Output voltage when LOW

Q2. Is it better to have a lower value of noise margin or a higher value?

A. A higher value of noise margin would be better.

Q3. Gate A has a greater propagation delay time than gate B. Which gate can operate at high frequency?

A. Gate B can operate at high frequency than gate A.

1-06-2021

Page #


Q4. How does excessive loading affect the noise margin of a gate?

A. Excessive loading reduces the noise margin of a gate.

 
## Section 15-2: CMOS

CMOS — Complementary Metal-Oxide Semiconductor

MOSFET — Metal-Oxide Semiconductor Field effect transistors.



n-channel

 

P-channel.

MOSFET Symbols



3-06-2021

Page #

### Section Checkups 15-2:

Q. What type of transistor is used in CMOS logic?

A. MOSFETs

Q. What is meant by the term Complementary?

A. Complementary is meant by there are two circuits n-type and p-type.

Q. Why must CMOS devices be handled with care?

A. Because electrostatic discharge can damage CMOS devices; electrostatic discharge is analog in nature so it can fuse both p-type and n-type circuits of CMOS/MOSFET.

### Section 15-3: TTL (Bipolar) Circuits.


TTL has totem-pole circuits

BJT- Bipolar Junction Transistor

BJT is an active switching element with npn and pnp terminals named: Base, emitter and collector.

3-08-2021

Page#

 

BJT (nnp)

Section ~~check~~ checkup 15-3:

Q. An npn BJT is on when the base is more negative than the emitter?

A. False, An npn BJT will be off.

Q. In terms of switching action, what do the on and off states of a BJT represent?

A. ~~What~~ On is ~~the~~ closed state and off is an open state.

Q. What are the two major types of output ~~ext~~ circuits in TTL?

A. Totem-pole and open-collector are types of TTL outputs.



3-06-2021

Page#

Q. Explain how tri-state logic differs from two-state logic?

A. Tri-state logic provides a high ~~st~~-impedance state, in which the output is disconnected from the rest of the circuit.

Section 15-4

Example 15-3:

Q. When a standard TTL NAND gate drives five TTL inputs, how much current does the driver output source, & much does it sink?

Total source current in HIGH output state:

$$I_{IH(max)} = 40 \mu A / \text{input}$$

$$I_{T(source)} = (5)(40 \mu) = 200 \mu A$$

$$I_{T(source)} = 200 \times 10^{-6} A$$

Ans.

Total sink current in (low output state):


$$I_{IL(max)} = -1.6 \text{ mA} / \text{input}$$

$$I_{T(sink)} = (5)(-1.6 \text{ mA}) = -8 \text{ mA} = -8 \times 10^{-3} A$$

3-06-2021

 Example 15-5:

Q. Write the output expression for the wired-AND configuration of open-collector AND gates in figure below:



A.  $X = ABCDEFGH$

4-wired 2-input AND gates  
creates an 8-input AND gate.

Related Problem:

Q. Determine the output expression if NAND gate is used.

A.

$$X = \overline{AB} \cdot \overline{CD} \cdot \overline{EF} \cdot \overline{GH}$$


4 wired 2-input NAND gates  
creates an AND gate with 4-2<sup>in</sup>-port  
NAND gates

3-06-2021

Page#

 Example 15-6:

Q. Three open collector AND gates are connected in a wired-AND configuration. Assume that the wired AND configuration as shown circuit is driving four standard TTL inputs ( $-1.6\text{mA}$  each).



(a) Write its expression

(b) Determine the minimum value of  $R_p$  if  $I_{OL(max)}$  for each gate is  $30\text{mA}$  and  $V_{OL(max)} = 0.4\text{V}$

(a)  $X = ABCDEF$

(b)  $R_p = \frac{V_{CC} - V_{OL(max)}}{I_{Rp}}$  ; Ohm's Law



3-06-2021

$$\therefore I_{Rp} = I_{OL(max)} - I_T$$

$$I_T = 4 \times 1.6 \text{ mA} = 6.4 \text{ mA} = 6.4 \times 10^{-3} \text{ A}$$

$$I_{Rp} = 30 \times 10^{-3} - 6.4 \times 10^{-3}$$

$$I_{Rp} = 23.6 \times 10^{-3} \text{ A}$$

Now,

$$R_p = \frac{V_{cc} - V_{OL(max)}}{I_{Rp}} = \frac{5 - 0.4}{2.3 \times 10^{-3}}$$

$$R_p = 295 \Omega$$


Ans.

Example 15-71

Q. Determine the value of the limiting Resistor,  $R_L$ , in the open-collector circuit if the LED current is to be 20 mA. Assume a 1.5 V drop across the LED when it is forward biased and a low state output voltage of 0.1 V at the output of the gate.

3-06-2021

Page #

 

Solution:

We use ohm's Law,

$$V_{R_L} = I R_L \Rightarrow R_L = \frac{V_{R_L}}{I}$$

$$V_{R_L} = V_{CC} - V_{L(\text{max})} - V_{OH(\text{max})}$$

$$= 5 - 1.5 - 0.1 = 3.4$$

$$V_{R_L} = 3.4 \text{ V}$$

$$R_L = \frac{V_{R_L}}{I} = \frac{3.4}{20 \times 10^{-3}} = 170 \Omega$$

Ans.

Related Problem:

Q. Determine  $R_L$  if LED requires 35 mA.

$$A. R_L = \frac{V_{R_L}}{I} = \frac{3.4}{35 \times 10^{-3}} = 97.143 \Omega$$

05-06-2021

Page #

## PROBLEMS

Q1. A certain logic gate has a  $V_{OH(min)}$  is 2.2V and it driving a gate with a  $V_{IH(min)} = 2.5V$ . Are these gates are compatible for HIGH-state operation? why?

A. These gates are not compatible for HIGH-state operations because  $V_{OH(min)} < V_{IH(min)}$ .

Q2. A certain Logic gate has a  $V_{OL(max)} = 0.45V$  and it is driving a gate with a  $V_{IL(max)} = 0.75V$ . Are these gates are compatible for Low-state operation? why?

A. The two gates are compatible for Low state operation because  $V_{OL(max)}$  is less than  $V_{IL(max)}$ .

Q3. A TTL gate has the following actual voltage level values:  $V_{IH(min)} = 2.25V$ ,  $V_{IL(max)} = 0.65V$ . Assuming it is being drive by a gate with  $V_{OH(min)} = 2.4V$  and  $V_{OL(max)} = 0.4V$ , What are the HIGH



05-06-2021

Page#

and low level noise margins?

A.


$$V_{NH} = V_{OH(min)} - V_{IH(min)}$$
$$= 2.4 - 2.25$$

$$V_{NH} = 0.25$$


$$V_{NL} = V_{IL(max)} - V_{OL(max)}$$
$$= 0.65 - 0.4$$

$$V_{NL} = 0.25$$

 
Q. Determine the state (on or off) of each MOSFET in Fig. 15-53.




ON

 

OFF

 





OFF

 

ON

05-6-2021

    Q16. Determine the BJT's in Fig. 15-55 are off and which are on?



Q23. Determine the minimum value for the pull up resistor in each circuit if  $I_{OL(max)} = 40\text{mA}$  and  $V_{OL(max)} = 0.25\text{V}$  for each gate assume that 10 standard TTL unit loads are being driven from output x and the supply voltage is 5V.

A. Data:

$$V_{OL(max)} = 0.25\text{V}$$

$$I_{OL(max)} = 40\text{mA} = 40 \times 10^{-3}\text{A}$$

$$V_{CC} = 5\text{V}$$

$$\therefore R_p = \frac{V_{CC} - V_{OL(max)}}{I_{Rp}}$$

$$\therefore I_{Rp} = I_{OL(max)} - I_T = 40 \times 10^{-3} - 10$$

$$I_{Rp} = -9.96\text{A}$$

$$R_p = \frac{5 - 0.25}{-9.96} =$$

$$R_p = -0.4769\Omega$$

Ans.



05-6-2021

Page #

Q25, Determine the IC family with the best speed-power product in Table 15-1.

A. ALVC

## CHAPTER # 4 MAVINO

### TTL CIRCUITS PROBLEMS

Q. A segment seven decoder is driving a LED display like. Which LEDs are on when digit 8 appears? Which LEDs are on when digit 4 appears?

A. For digit 8, all LEDs are on i.e. a, b, c, d, e and f.

For digit 4, b, c, f and g are on.

Q. What is propagation delay?

A. Propagation delay is the length of time required for a signal to reach its destination.

05-06-2021

Page#



Q. What is the noise margin of TTL Devices?

A. Standard TTL devices has noise margin of ~~0.4V~~ 0.4V



2-6 (Vi): Solid State Circuit

Transforming from Logic Map:

Transistor Inverter:

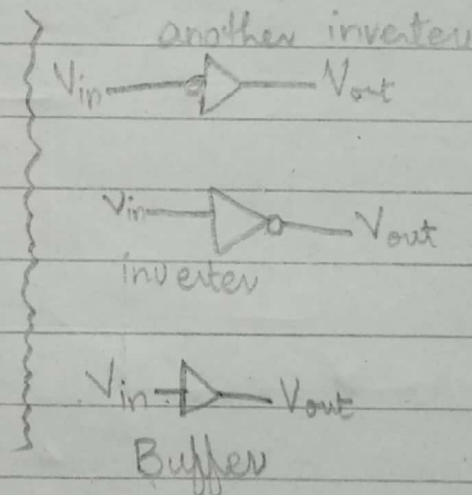 


Diode OR Gate:

  


05-06-2021

Page#

### Diode AND Gate:

 

### Standard TTL Inverter:

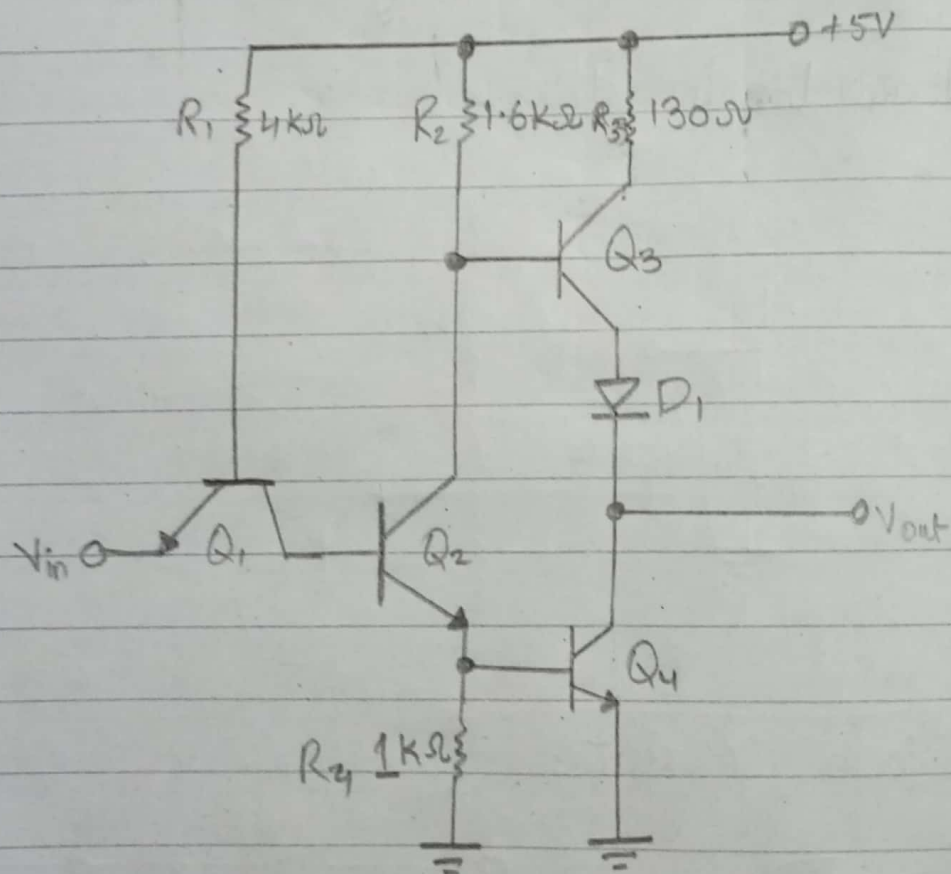




06-06-2021

Page#


Standard TTL NAND gate:

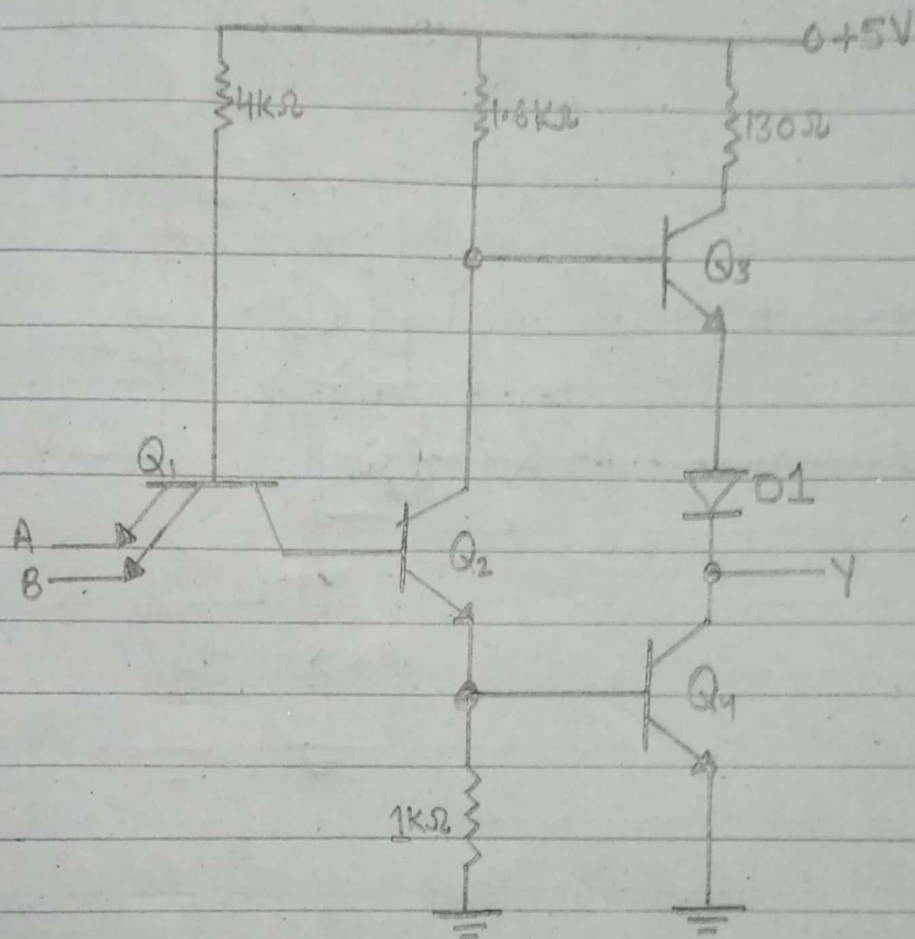


06-06-2021

Page #

## Standard TTL NOR Gate :

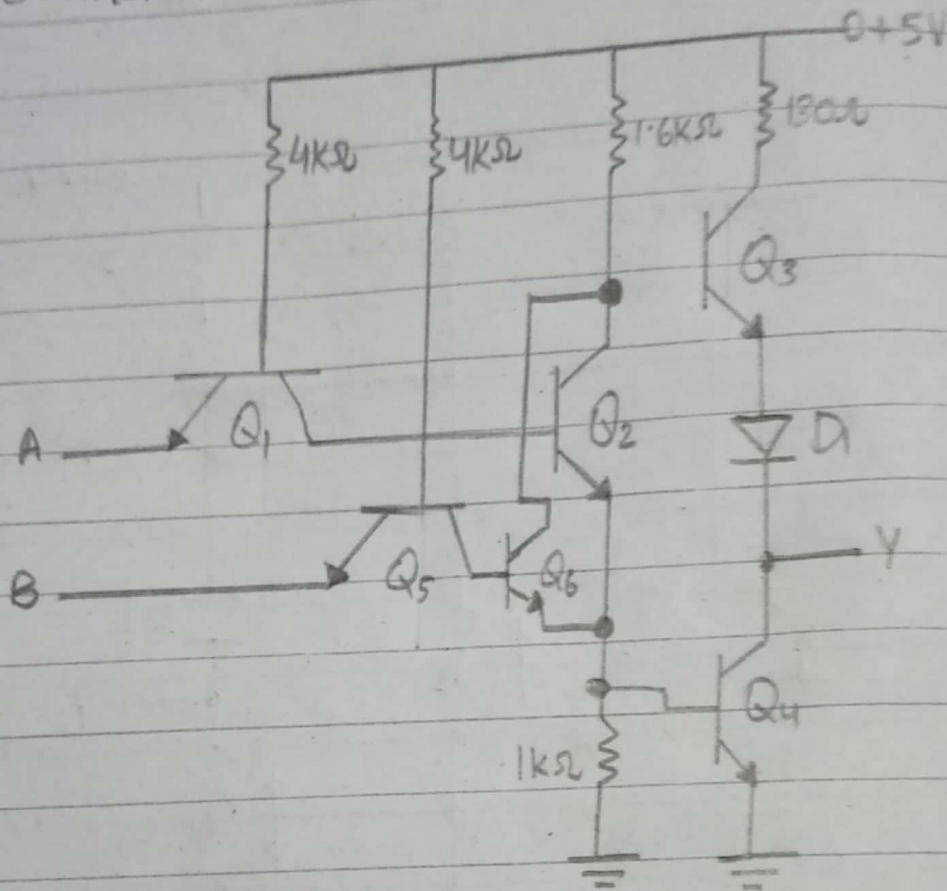

 Q. Transform the given Logic Map to simple TTL/DDL Logic based solid-state circuit.



$$Y = (\bar{A} + B) \cdot (C + D)$$

Solution:

